
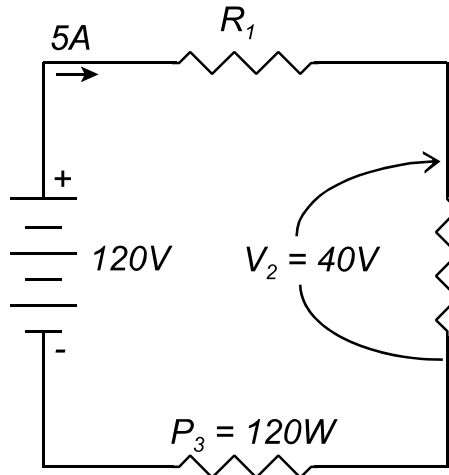


**ELECTROTECHNOLOGY
ELTK1100
ASSIGNMENT #4**


1. Find the Unknown Resistances.

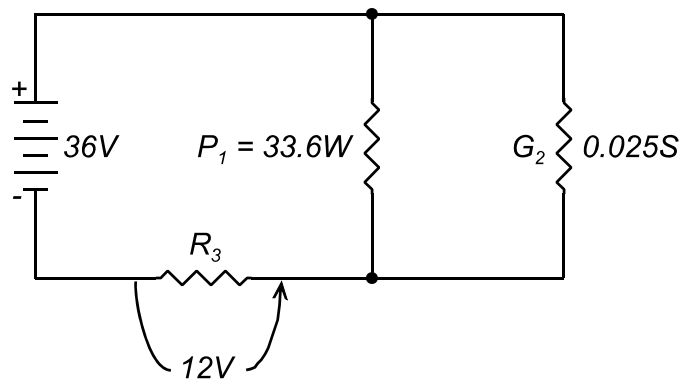


2. Find the Unknown Resistances.



3. Find the Unknown Resistances.

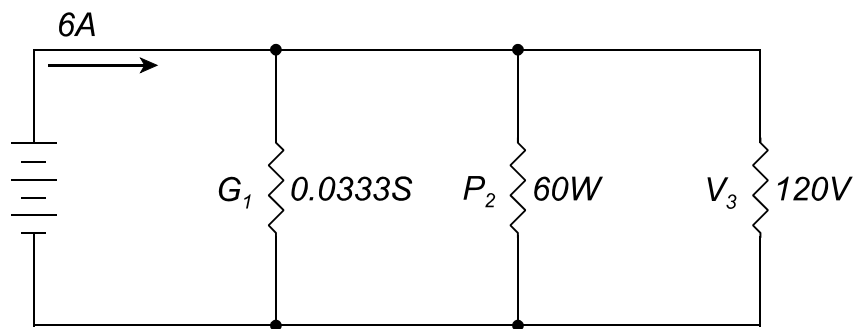

4. Find the Unknown Resistances.

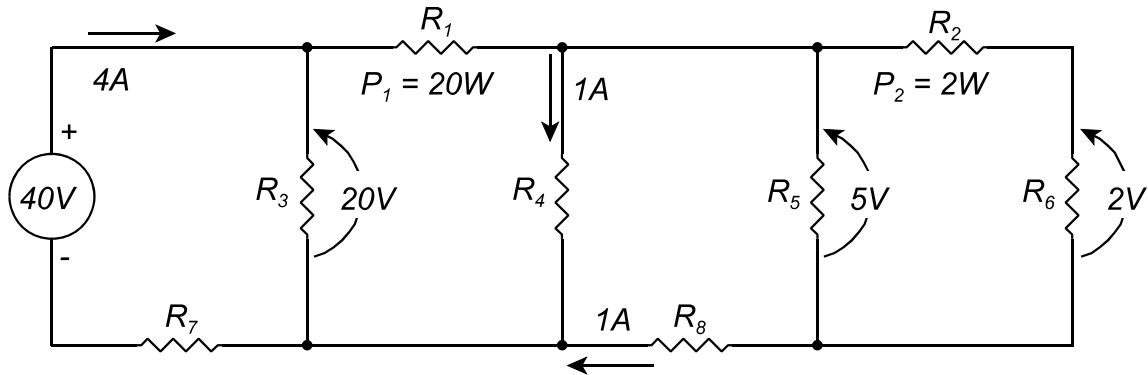


5. How much current will flow through a wire supplying a 1.5 hp motor at 120V? How much will it cost to run this motor for 8 h/day for 50 days if energy costs 6¢/kW-h?
6. An oven heating element on an electric range operating on 240V has a resistance of 6Ω . How much current does it draw? What is the power rating for this element? How much will it cost, if the element is on for 6 hours and energy costs 6¢/kW-h?
7. A 50 bulb set of series connected, Xmas mini-lights consumes 25W of power from a 120V source. Determine:
- the power delivered to each bulb.
 - the voltage drop across each bulb.
 - the resistance of each bulb.
 - the cost to operate these lights for 6 hrs/day for the 12 days of Xmas, if electrical energy costs \$0.08/kWh.
8. For the circuit of Question 7, if a single bulb were to become an open circuit, the entire string would stop working. To prevent this from occurring, each light bulb has a small metal strip which shorts the light bulb when the filament fails.


If two light bulbs fail, what would be the effect on the rest of the bulbs?

- they would be off.
- they would be brighter.
- they would be dimmer.
- they would be the same intensity.

Reason out your answer.

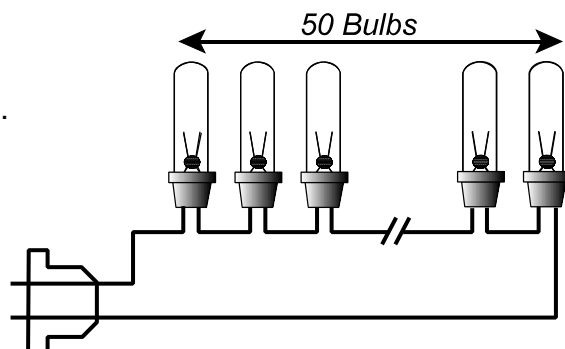

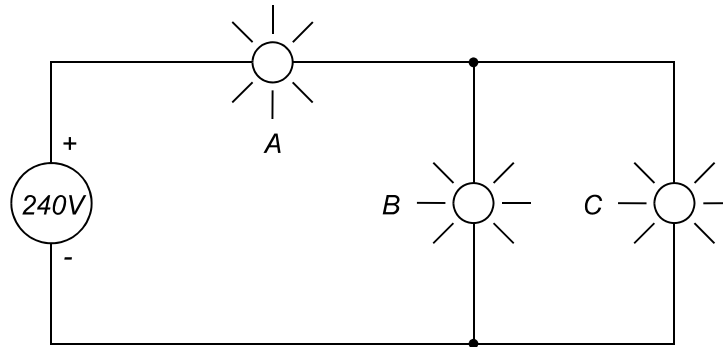9. Three identical light bulbs (A, B & C) are connected as shown. When the power is turned on, the brightness of light bulb A will be:
- dimmer than light bulb B.
 - equal in brightness to light bulb B.
 - brighter than light bulb B.
- Reason out your answer.



10. If the light bulbs for Question 9 have a resistance of 240Ω and are rated at 60W, explain the operation of the circuit when the power is applied.
11. Assuming a rate of \$0.06 per kW-h, determine the cost of operating the following electrical equipment for 30 days:
- 1.2 kW iron for 45 minutes/day.
 - 2 hp motor for 5 h/day.
 - one 300 W, four 100 W, two 60 W and six 40 W lamps for 6 h/day.
 - 750 W microwave for 30 minutes/day.
12. A 120V outlet is protected by a 25A circuit breaker. A 700W toaster, an 800W coffee maker and a 900W microwave oven are already operating from this outlet. Can you plug in a 1000W hair dryer without tripping the circuit breaker?
13. 1 kg. of a liquid with a specific heat of 0.8, is to have it's temperature raised from 10°C to 50°C . How long will it take if the heating element is rated for 240V, 8A and the efficiency is 75%? What would be the temperature of this liquid, if it was left on the heating element for 2 minutes?
14. It costs a manufacturer \$20.00 to heat a mass of water from 25°C to 100°C in 5 hours for his production line. Energy costs 8¢/kW-h. The water heater is rated at 480V and it's efficiency is 75%. What current flows? What is the mass of water heated?
15. A 10Ω heating element operates from a 580V source. It takes 20 minutes to heat 100 kg. of water from 20°C to boiling point, what is the efficiency of heat transfer.