

# Table of Contents

Experiment 1:	Resistors	1
Experiment 2:	Ohm's Law	11
Experiment 3:	Series Circuits - Kirchhoff's Voltage Law	21
Experiment 4:	Parallel Circuits - Kirchhoff's Current Law	31
Experiment 5:	Series/Parallel Circuits	41
Experiment 6:	Kirchhoff's Laws and Series/Parallel Circuits	51
Experiment 7:	Voltage Dividers	57
Experiment 8:	Voltmeter Design and Voltmeter Loading	67

# Parts List

	1	2	3	4	5	6	7	8
120Ω, 1W							✓	
250Ω, 1W							✓	
330Ω			✓			✓		
360Ω, 1W							✓	
470Ω			✓			✓		
500Ω, 5W							✓	
560Ω		✓			✓	✓		
560Ω, 1W							✓	
820Ω					✓			
1kΩ			✓	✓	✓		✓	2
1.2kΩ			✓	✓	✓	✓		
2.2kΩ				✓	✓	✓		
3.3kΩ				✓	✓	✓		
4.7kΩ						✓		
10kΩ								2
100kΩ								2
5kΩ/10kΩ Potentiometer	✓	✓						
Ohmmeter	✓	✓	✓	✓	✓	✓		
Ammeter		✓	✓	✓	✓	✓	✓	
Voltmeter		✓	✓	✓	✓	✓	✓	✓
DMM								✓
1 mA, 100Ω Meter Movement								✓
Decade Box								✓
Max Voltage		16	24	12	24	30	21	16
Pre-Lab Calculations		✓			✓	✓	✓	