

ELTK1100 FORMULAS

Ohm's Law

$$I = \frac{V_T}{R}$$

Voltage Drop

$$V_x = I_x * R_x$$

Current

$$I = \frac{q}{t}$$

$$1 \text{ C} = 6.25 * 10^{18} \text{ electrons}$$

Power

$$P = V_T I = I^2 R = \frac{V_T^2}{R}$$

$$1 \text{ hp} = 746 \text{ W}$$

Energy

$$\text{Energy} = P t$$

$$\text{Cost} = \text{Energy} * \frac{\text{cost}}{\text{kW}\cdot\text{h}}$$

P in kW t in h Energy in kW•h

Heat

$$Q = M C \Delta T \quad \Delta T = T_2 - T_1$$

$$\text{Efficiency} = \frac{Q}{\text{Heat Produced}} * 100\%$$

$$\text{Heat Produced} = \frac{P t}{4.187}$$

P in W t in s

Series circuits (sub-circuits)

$$I_T = I_1 = I_2 = I_3 = \dots$$

$$R_T = R_1 + R_2 + R_3 + \dots$$

$$I_T = \frac{V_T}{R_T}$$

KVL

$$V_T = V_1 + V_2 + V_3 + \dots$$

Voltage Division (for series resistors)

$$V_x = \frac{R_x}{R_T} * V_T$$

Parallel circuits (sub-circuits)

$$V_T = V_1 = V_2 = V_3 = \dots$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

$$I_T = \frac{V_T}{R_T}$$

KCL

$$I_T = I_1 + I_2 + I_3 + \dots$$

Current Division (for parallel resistors)

$$I_x = \frac{R_{eq}}{R_x} * I_T$$

Current Division (for 2 parallel resistors)

$$I_x = \frac{\text{Opposite}}{\text{Sum}} * I_T$$

Two resistors in parallel

$$R_1 \parallel R_2 = \frac{R_1 * R_2}{(R_1 + R_2)}$$

n equal resistors in parallel

$$R_T = \frac{R}{n}$$

Conductance

$$G = \frac{1}{R}$$

$$G_T = G_1 + G_2 + G_3 + \dots$$

$$I_T = V_T G_T$$

Conductor Resistance

$$R = \frac{\rho \ell}{A}$$

Metric

English

$$1 \text{ mil} = 0.001''$$

$$A = \frac{\pi d^2}{4}$$

$$A = d^2$$

$$1 \text{ CM} = 1 \text{ mil}^2$$

Effect of Temperature on Resistance

$$R_{T_2} = \frac{(1 + \alpha_0 T_2)}{(1 + \alpha_0 T_1)} * R_{T_1}$$

$$R_T = (1 + \alpha_0 T) * R_0$$

Magnetomotive Force

$$F_M = N I$$

Magnetic Flux

$$\phi = \frac{F_M}{R_M}$$

Dynamic Induction

$$V_{IND} = N B \ell v$$

Static Induction

$$V_{IND} = N \frac{\Delta \phi}{\Delta t} \quad \Delta \phi = \phi_1 - \phi_2$$

Inductance

$$L = \frac{N^2}{R_M}$$

$$V_{IND} = L \frac{\Delta I}{\Delta t} \quad \Delta I = I_1 - I_2$$

Series $L_T = L_1 + L_2 + L_3 + \dots$

Parallel $\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots$

Error

$$\% \text{ Error} = \left| \frac{\text{Actual} - \text{Measured}}{\text{Actual}} \right| * 100\%$$

Battery Capacity

$$\text{Capacity} = \text{Discharge Rate} * \text{time}$$

Batteries

Series $E_T = S E \quad r_T = S r$

Parallel $E_T = E \quad r_T = \frac{r}{P}$

Series/Parallel $E_T = S E \quad r_T = \frac{S r}{P}$

$$V_T = E_T - I_T r_T$$