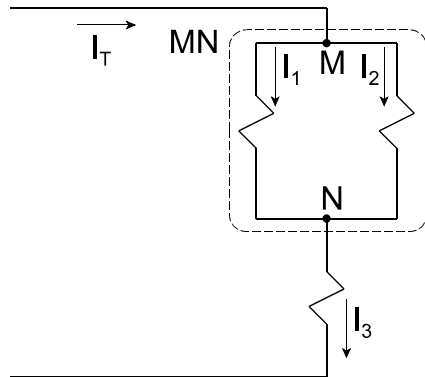


**ELECTROTECHNOLOGY  
ELTK1100  
ASSIGNMENT #3  
SOLUTIONS  
(Current Division)**

---

1.



$$I_1 = \frac{R_{MN}}{R_1} * I_T$$

$$= \frac{1.5k\Omega}{2k\Omega} * 21.8mA = 16.3mA. \quad 3$$


$$I_2 = \frac{R_{MN}}{R_2} * I_T$$

$$= \frac{1.5k\Omega}{6k\Omega} * 21.8mA = 5.5mA. \quad 4$$

$$R_1 \parallel R_2 = 2k\Omega \parallel 6k\Omega = \frac{2 * 10^3 * 6 * 10^3}{(2 * 10^3 + 6 * 10^3)}$$

$$= \frac{1.2 * 10^7}{8 * 10^3} = 1.5k\Omega = R_{MN}$$
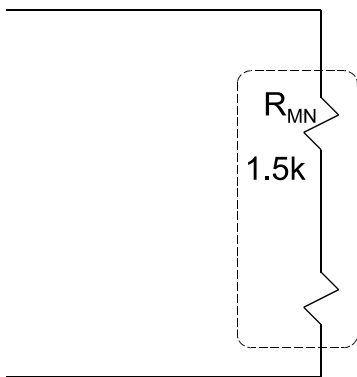
<i>Check</i> 16.3 + 5.5 = 21.8
--------------------------------



	V (V)	I (mA)	R (Ω)
T	120	21.8 <sup>2</sup>	5.5k <sup>1</sup>
1	32.7 <sup>5</sup>	16.3 <sup>3</sup>	2k
2	32.7 <sup>6</sup>	5.5 <sup>4</sup>	6k
3	87.3 <sup>7</sup>	21.8 <sup>2</sup>	4k

$$R_{MN} \text{ s } R_3 = 1.5k\Omega \text{ s } 4k\Omega = 1.5k\Omega + 4k\Omega = 5.5k\Omega$$

$$R_T = 5.5k\Omega \quad 1$$

$$I_T = \frac{V_T}{R_T} = \frac{120V}{5500\Omega} = 21.8mA. \quad 2$$


$$V_1 = I_1 R_1 = 16.3mA * 2k\Omega$$

$$= 16.3 * 10^{-3} * 2 * 10^3 = 32.7V. \quad 5$$

$$V_2 = I_2 R_2 = 5.5mA * 6k\Omega = 32.7V. \quad 6$$


$$V_3 = I_3 R_3 = 21.8mA * 4k\Omega = 87.3V. \quad 7$$

2.

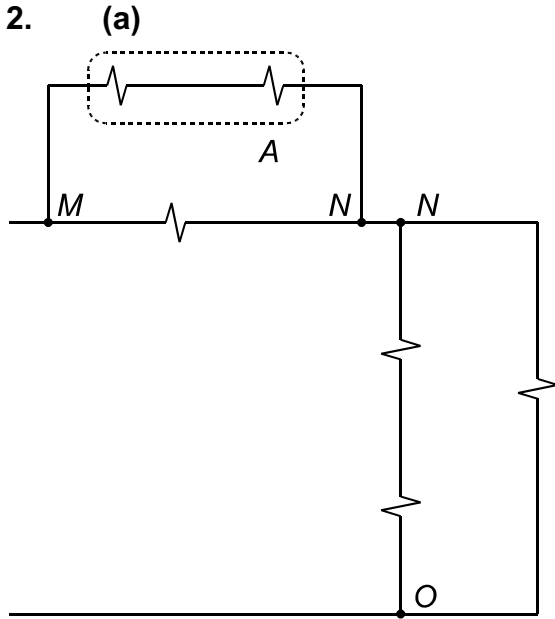

	V (V)	I (mA)	R ( $\Omega$ )
T	12	75 <sup>2</sup>	160 <sup>1</sup>
1	1	62.5 <sup>5</sup>	16
2	3.5	62.5 <sup>5</sup>	56
3	4.5	12.5 <sup>6</sup>	360
4	5	33.3 <sup>3</sup>	150
5	2.5 <sup>7</sup>	33.3 <sup>3</sup>	75
6	7.5	41.7 <sup>4</sup>	180

$$R_1 s R_2 = 16 s 56 = 72 = R_A$$

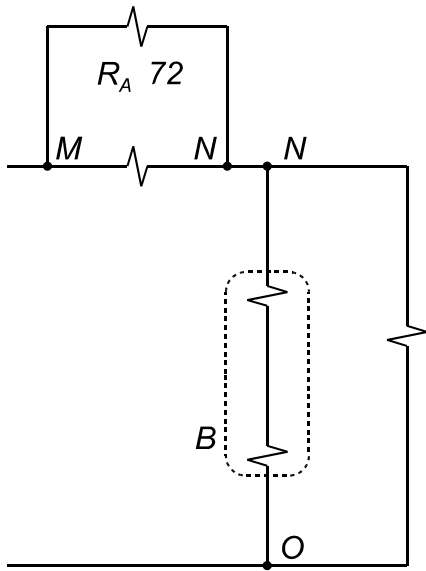


$$R_4 s R_5 = 150 s 75 = 225 = R_B$$

(e)

$$V_5 = I_5 * R_5$$
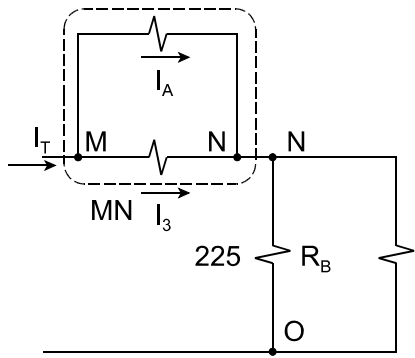
$$= 33.3 \text{ mA} * 75 \Omega = 2.5 \text{ V}^7$$



(c)(d)

$$I_1 = I_2 = I_A = \frac{R_{MN}}{R_A} * I_T$$


$$= \frac{60\Omega}{72\Omega} * 75mA = 62.5mA \quad 5$$

$$I_3 = \frac{R_{MN}}{R_3} * I_T$$

$$= \frac{60\Omega}{360\Omega} * 75mA = 12.5mA \quad 6$$

$$R_A \parallel R_3 = 72 \parallel 360 = \frac{72 * 360}{(72 + 360)} = 60 = R_{MN}$$

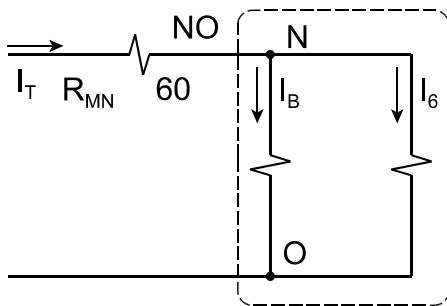Check $62.5 + 12.5 = 75$
--------------------------



$$I_4 = I_5 = I_B = \frac{R_{NO}}{R_B} * I_T$$


$$= \frac{100\Omega}{225\Omega} * 75mA = 33.3mA \quad 3$$

$$I_6 = \frac{R_{NO}}{R_6} * I_T$$

$$= \frac{100\Omega}{180\Omega} * 75mA = 41.7mA \quad 4$$

$$R_B \parallel R_6 = 225 \parallel 180 = \frac{225 * 180}{(225 + 180)} = 100 = R_{NO}$$

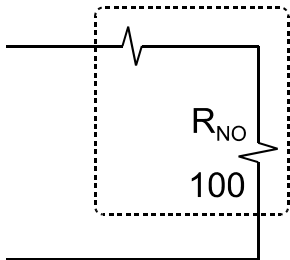Check $33.3 + 41.7 = 75$
--------------------------




$$R_{MN} \text{ s } R_{NO} = 60 \text{ s } 100 = 160$$

$$R_T = 160\Omega \quad 1$$

(b)

$$I_T = \frac{V_T}{R_T} = \frac{12V}{160\Omega} = 75mA. \quad 2$$

3. (a)

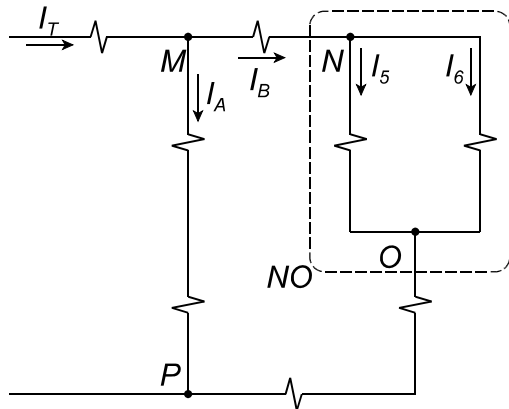

$$I_5 = \frac{R_{NO}}{R_5} * I_B$$


$$= \frac{235\Omega}{470\Omega} * 30.9mA = 15.5mA \quad ^5$$

$$I_6 = 15.5mA \quad ^6 \text{ equal resistors in parallel}$$

Check  $15.5 + 15.5 = 31.0$

Difference due to rounding

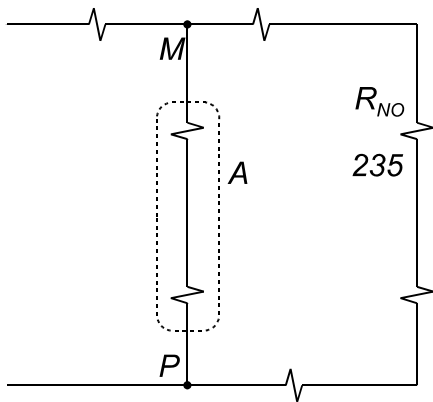
$$R_5 \parallel R_6 = 470 \parallel 470 = \frac{470}{2} = 235 = R_{NO}$$



(d)  $V_4 = I_4 * R_4$   
 $= 34.0mA * 560\Omega = 19.0V \quad ^7$

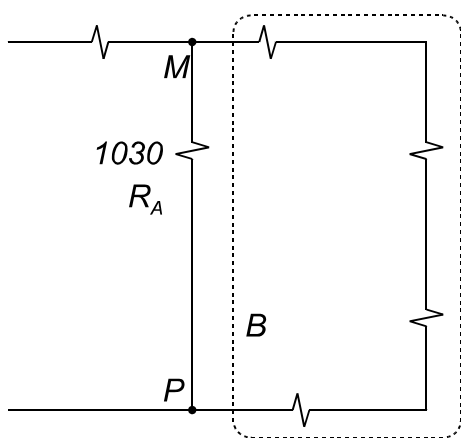
(c)  $V_5 = I_5 * R_5$   
 $= 15.5mA * 470\Omega = 7.29V \quad ^8$

$$R_3 \text{ s } R_4 = 470 \text{ s } 560 = 1030 = R_A$$




$$R_2 \text{ s } R_{NO} \text{ s } R_7 \text{ s } R_8 = 330 \text{ s } 235 \text{ s } 470 \text{ s } 100 = 1135 = R_B$$

	V (V)	I (mA)	R (Ω)
T	100	64.9 <sup>2</sup>	1.54k <sup>1</sup>
1	64.9	64.9 <sup>2</sup>	1k
3	16	34.0 <sup>3</sup>	470
4	19.0 <sup>7</sup>	34.0 <sup>3</sup>	560
2	10.2	30.9 <sup>4</sup>	330
7	14.5	30.9 <sup>4</sup>	470
8	3.09	30.9 <sup>4</sup>	100
5	7.29 <sup>8</sup>	15.5 <sup>5</sup>	470
6	7.29	15.5 <sup>6</sup>	470

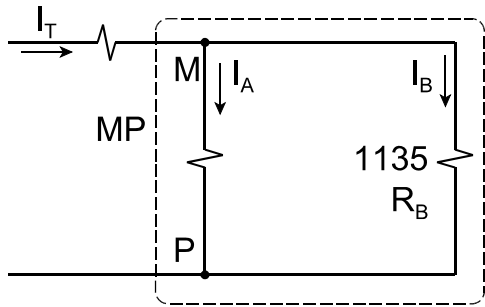
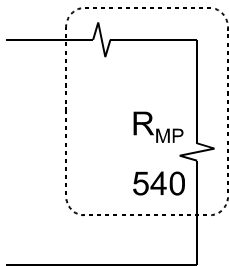
$$R_A \parallel R_B = 1030 \parallel 1135 = 540 = R_{MP}$$



$$R_1 \text{ s } R_{MP} = 1k \text{ s } 540 = 1.54k$$

$$R_T = 1.54k\Omega \quad 1$$

(b)

$$I_T = \frac{V_T}{R_T} = \frac{100V}{1.54k\Omega} = 64.9mA \quad 2$$

4.

$$I_T = 0.02A = 20mA$$

From KCL

$$I_T = I_1 + I_2$$

$$\therefore I_2 = I_T - I_1 = 20mA - 16mA$$

$$= 4mA \quad 1$$

$$R_1 \text{ is parallel with } R_2, \therefore V_1 = V_2 = 20V \quad 2$$

From KVL

$$V_T = V_1 + V_3 \text{ or}$$

$$V_T = V_2 + V_3$$

$$V_T = 20V + 16V = 36V \quad 3$$

(e)


$$I_3 = I_4 = I_A = \frac{R_{MP}}{R_A} * I_T$$

$$= \frac{540\Omega}{1030\Omega} * 64.9mA = 34.0mA \quad 3$$

$$I_2 = I_7 = I_8 = I_B = \frac{R_{MP}}{R_B} * I_T$$

$$= \frac{540\Omega}{1135\Omega} * 64.9mA = 30.9mA \quad 4$$

Check  $34.0 + 30.9 = 64.9$

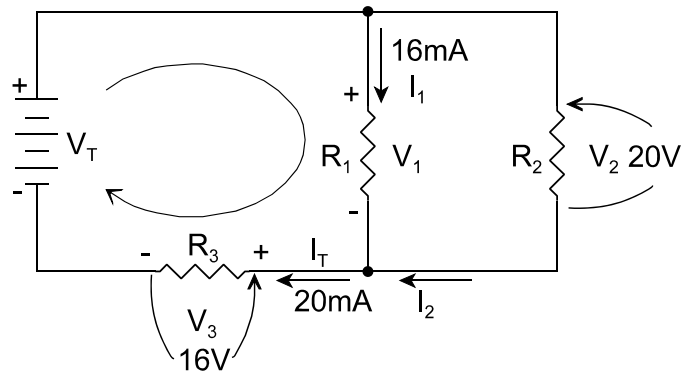

$$R_T = \frac{V_T}{I_T} = \frac{36V}{20mA} = 1800\Omega \quad 4$$

$$R_1 = \frac{V_1}{I_1} = \frac{20V}{16mA} = 1250\Omega \quad 5$$


$$R_2 = \frac{V_2}{I_2} = \frac{20V}{4mA} = 5000\Omega \quad 6$$

$$R_3 = \frac{V_3}{I_3} = \frac{16V}{20mA} = 800\Omega \quad 7$$


	V (V)	I (mA)	R ( $\Omega$ )
T	36 <sup>3</sup>	20	1800 <sup>4</sup>
1	20 <sup>2</sup>	16	1250 <sup>5</sup>
2	20	4 <sup>1</sup>	5000 <sup>6</sup>
3	16	20	800 <sup>7</sup>

Check  $1250 \parallel 5000 = 1000$   
 $1000 \text{ s } 800 = 1800$

5. (a)

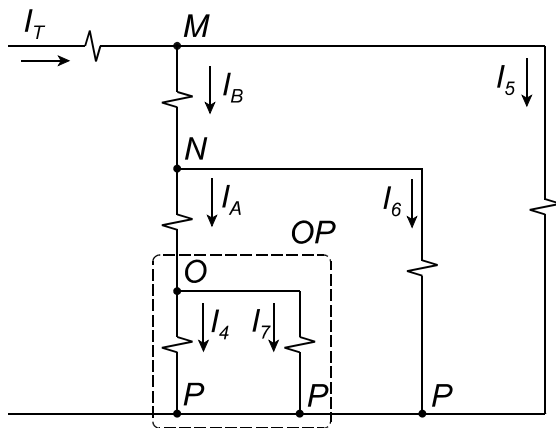
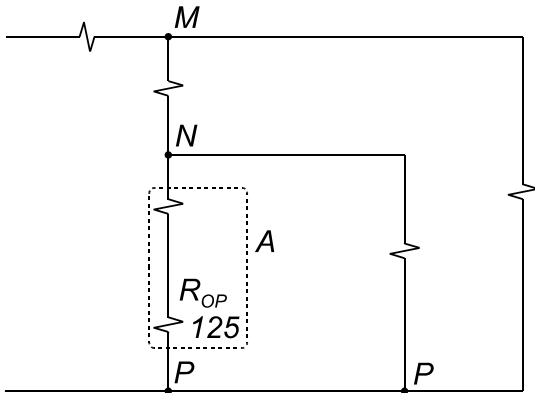
$$R_4 \parallel R_7 = 150 \parallel 750 = 125 = R_{OP}$$



$$R_3 \text{ s } R_{OP} = 200 \text{ s } 125 = 325 = R_A$$

(d)


$$I_4 = \frac{R_{OP}}{R_4} * I_A$$

$$= \frac{125\Omega}{150\Omega} * 144mA = 120mA \quad 7$$


$$I_7 = \frac{R_{OP}}{R_7} * I_A$$

$$= \frac{125\Omega}{750\Omega} * 144mA = 24mA \quad 8$$


Check  $120 + 24 = 144$

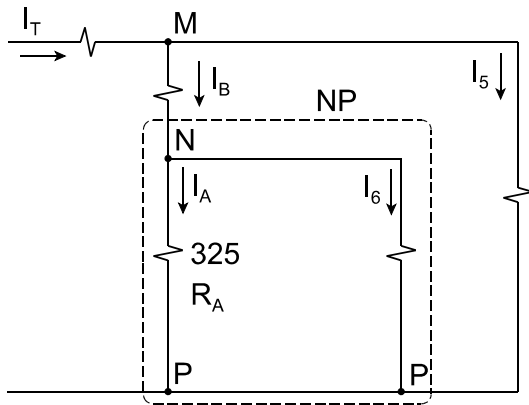
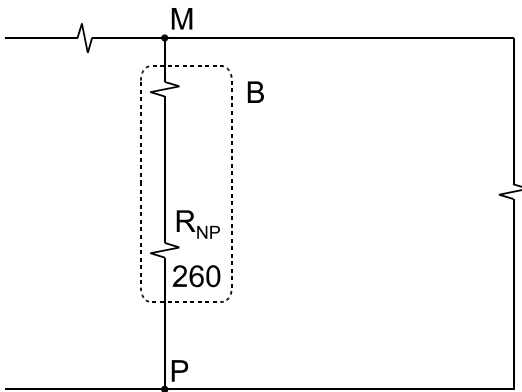
$$R_A \parallel R_6 = 325 \parallel 1.3k = 260 = R_{NP}$$


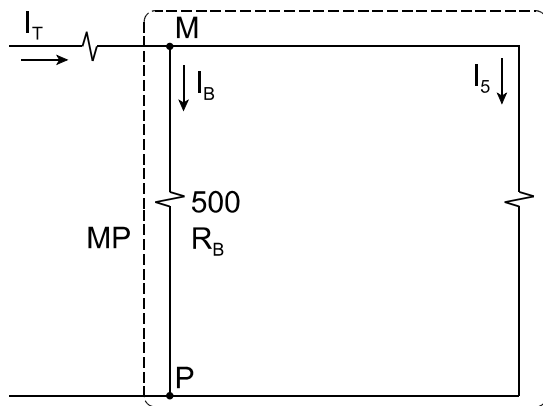
$$R_2 \text{ s } R_{NP} = 240 \text{ s } 260 = 500 = R_B$$



$$R_B \parallel R_5 = 500 \parallel 750 = 300 = R_{MP}$$

(d)

$$I_3 = I_A = \frac{R_{NP}}{R_A} * I_B$$

$$= \frac{260 \Omega}{325 \Omega} * 180 \text{ mA} = 144 \text{ mA} \quad 5$$

$$I_6 = \frac{R_{NP}}{R_6} * I_B$$

$$= \frac{260 \Omega}{1.3 \text{ k}\Omega} * 180 \text{ mA} = 36 \text{ mA} \quad 6$$

Check	$144 + 36 = 180$
-------	------------------

(d)


$$I_2 = I_B = \frac{R_{MP}}{R_B} * I_T$$

$$= \frac{300 \Omega}{500 \Omega} * 300 \text{ mA} = 180 \text{ mA} \quad 3$$

$$I_5 = \frac{R_{MP}}{R_5} * I_T$$

$$= \frac{300 \Omega}{750 \Omega} * 300 \text{ mA} = 120 \text{ mA} \quad 4$$

Check	$180 + 120 = 300$
-------	-------------------

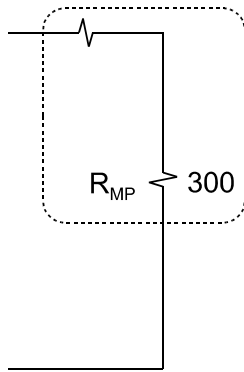

$$R_1 \text{ s } R_{MP} = 100 \text{ s } 300 = 400$$

$$R_T = 400 \Omega^1$$

(b)

$$I_T = \frac{V_T}{R_T} = \frac{120 \text{ V}}{400 \Omega} = 300 \text{ mA}^2$$

(c)

$$V_7 = I_7 * R_7 = 24 \text{ mA} * 750 \Omega = 18 \text{ V}^9$$

$$V_6 = I_6 * R_6 = 36 \text{ mA} * 1.3 \text{ k}\Omega = 46.8 \text{ V}^{10}$$

$$V_5 = I_5 * R_5 = 120 \text{ mA} * 750 \Omega = 90 \text{ V}^{11}$$

	V (V)	I (mA)	R ( $\Omega$ )
<b>T</b>	<b>120</b>	300 <sup>2</sup>	400 <sup>1</sup>
<b>1</b>	30	300 <sup>2</sup>	<b>100</b>
<b>5</b>	90 <sup>11</sup>	120 <sup>4</sup>	<b>750</b>
<b>2</b>	43.2	180 <sup>3</sup>	<b>240</b>
<b>6</b>	46.8 <sup>10</sup>	36 <sup>6</sup>	<b>1.3k</b>
<b>3</b>	28.8	144 <sup>5</sup>	<b>200</b>
<b>7</b>	18 <sup>9</sup>	24 <sup>8</sup>	<b>750</b>
<b>4</b>	18	120 <sup>7</sup>	<b>150</b>

6.

This problem exercises the rules for series/parallel circuits.

The information in **Bold** and *Italics* on the VIR chart indicates what is given.

$$G_5 = 0.5 \text{ S}$$

$$R_5 = \frac{1}{G_5} = \frac{1}{0.5 \text{ S}} = 2 \Omega^1$$

$$I_1 = I_7 = I_T = 8 \text{ A}^2$$

This is obvious since they are in series with source.

Similarly


$$I_2 = I_6 = 5 \text{ A}^3$$

By KCL on Node M

$$I_7 = I_6 + I_8$$

$$\therefore I_8 = I_7 - I_6 = 8 \text{ A} - 5 \text{ A} = 3 \text{ A}^4$$

	V (V)	I (A)	R ( $\Omega$ )
<b>T</b>	<b>120</b>	<b>8</b>	15
<b>1</b>	<b>20</b>	8 <sup>2</sup>	2.5 <sup>9</sup>
<b>7</b>	40 <sup>5</sup>	8 <sup>2</sup>	<b>5</b>
<b>8</b>	60 <sup>5</sup>	3 <sup>4</sup>	<b>20</b>
<b>2</b>	10 <sup>5</sup>	5 <sup>3</sup>	<b>2</b>
<b>6</b>	20 <sup>6</sup>	<b>5</b>	4 <sup>9</sup>
<b>9</b>	<b>30</b>	2 <sup>8</sup>	15 <sup>9</sup>
<b>3</b>	<b>9</b>	3 <sup>7</sup>	<b>3</b>
<b>4</b>	<b>15</b>	3 <sup>7</sup>	5 <sup>9</sup>
<b>5</b>	6	3 <sup>7</sup>	2 <sup>1</sup>

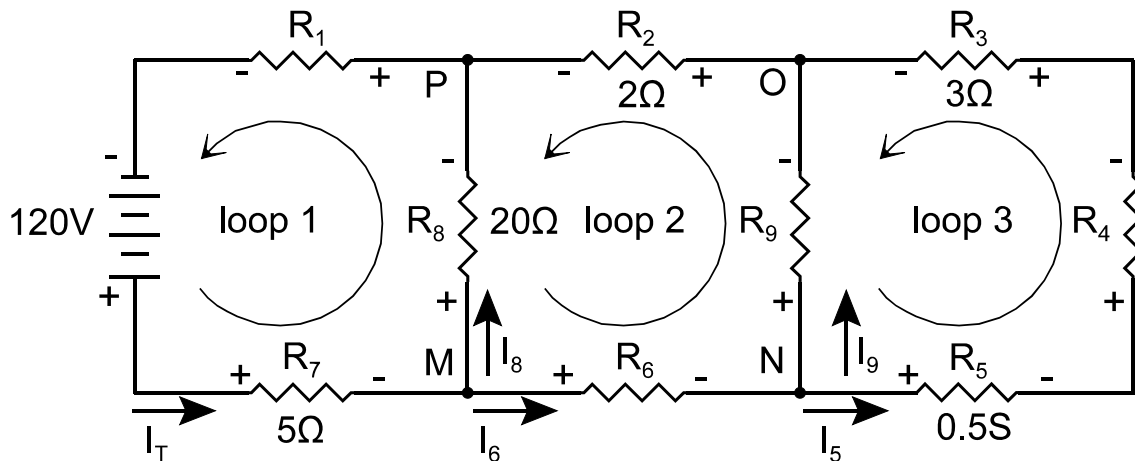

You know the current and resistance for  $R_7$ ,  $R_8$  and  $R_2$ ,  $\therefore$  you can work out their voltage drops.

$$V_7 = I_7 * R_7 = 8A * 5\Omega = 40V \quad 5$$

$$V_8 = I_8 * R_8 = 3A * 20\Omega = 60V$$

$$V_2 = I_2 * R_2 = 5A * 2\Omega = 10V$$

From KVL loop 1

$$+V_T - V_1 - V_8 - V_7 = 0$$

$$V_1 + V_8 + V_7 = V_T$$

$$20V + 60V + 40V = 120V$$

$R_1$  and  $R_7$  consume  $20V + 40V$  of potential since they are in series with the source. The left over potential  $60V$  is available for the rest of the circuit in parallel.

From KVL loop 2

$$+V_8 - V_2 - V_9 - V_6 = 0$$

$$V_6 = V_8 - V_2 - V_9 = 60V - 10V - 30V = 20V \quad 6$$

By Ohms Law

$$I_3 = I_4 = I_5 = \frac{V_3}{R_3} = \frac{9V}{3\Omega} = 3A \quad 7$$

By KCL on Node N

$$I_6 = I_5 + I_9$$

$$\therefore I_9 = I_6 - I_5 = 5A - 3A = 2A \quad 8$$


$$R_1 = \frac{V_1}{I_1} = \frac{20V}{8A} = 2.5\Omega \quad 9$$

$$R_6 = \frac{V_6}{I_6} = \frac{20V}{5A} = 4\Omega$$


$$R_9 = \frac{V_9}{I_9} = \frac{30V}{2A} = 15\Omega$$

$$R_4 = \frac{V_4}{I_4} = \frac{15V}{3A} = 5\Omega$$


7. (a)

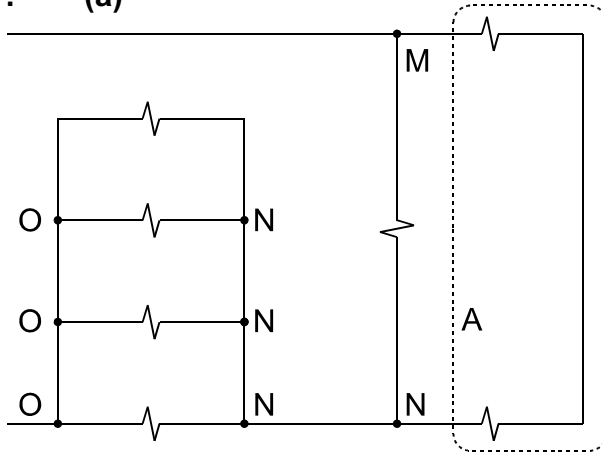
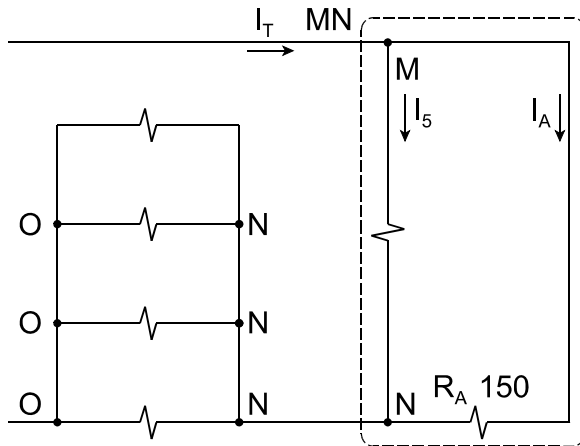
$$R_6 \text{ s } R_7 = 68 \text{ s } 82 = 150 = R_A$$


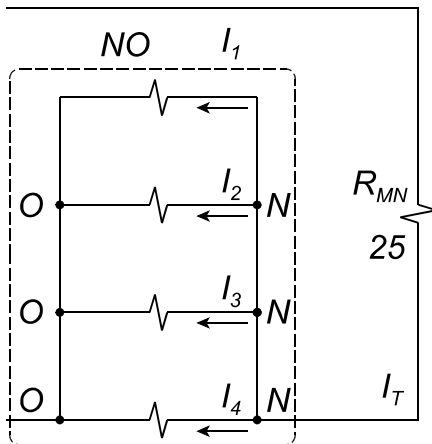
$$R_5 \parallel R_A = 30 \parallel 150 = 25 = R_{MN}$$



$$R_1 \parallel R_2 \parallel R_3 \parallel R_4 = 180 \parallel 180 \parallel 20 \parallel 180 = 15 = R_{NO}$$

or

$$180 \parallel 180 \parallel 180 = 30$$

$$30 \parallel 20 = 15 = R_{NO}$$

$$I_5 = \frac{R_{MN}}{R_5} * I_T$$

$$= \frac{25\Omega}{30\Omega} * 2A = 1.667A \quad 5$$

$$I_6 = I_7 = I_A = \frac{R_{MN}}{R_A} * I_T$$

$$= \frac{25\Omega}{150\Omega} * 2A = 0.333A \quad 6$$

Check	$1.667 + 0.333 = 2$
-------	---------------------

(d)

$$I_1 = I_2 = I_4 = \frac{R_{NO}}{R_1} * I_T$$


$$= \frac{15\Omega}{180\Omega} * 2A = 0.167A \quad 3$$

$$I_3 = \frac{R_{NO}}{R_3} * I_T$$

$$= \frac{15\Omega}{20\Omega} * 2A = 1.5A \quad 4$$

Check	$0.167 + 0.167 + 1.5 + 0.167 = 2$
-------	-----------------------------------

Use reciprocal rule

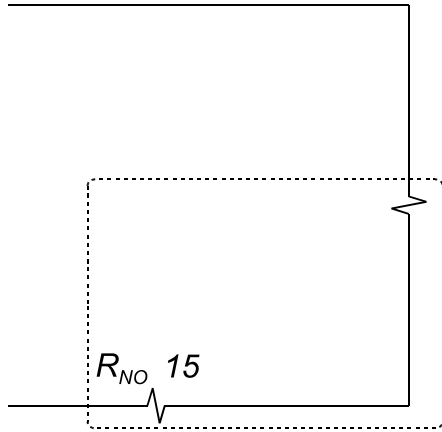

	V (V)	I (A)	R (Ω)
T	80 <sup>2</sup>	2	40 <sup>1</sup>
1	30	0.167 <sup>3</sup>	180
2	30	0.167 <sup>3</sup>	180
3	30	1.5 <sup>4</sup>	20
4	30	0.167 <sup>3</sup>	180
5	50	1.667 <sup>5</sup>	30
6	22.6 <sup>6</sup>	0.333 <sup>6</sup>	68
7	27.3	0.333 <sup>6</sup>	82

$$R_{NO} \text{ s } R_{MN} = 15 \text{ s } 25 = 40$$


$$R_T = 40 \Omega^1$$

(b)

$$V_T = I_T * R_T = 2A * 40 \Omega = 80V^2$$

$$(c) V_6 = I_6 * R_6 = 0.333A * 68 \Omega = 22.6V^7$$

8. (a)

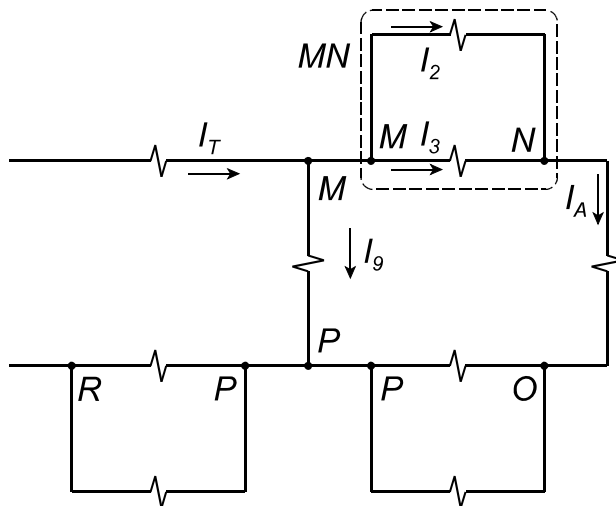

(c)

$$I_2 = \frac{R_{MN}}{R_2} * I_A$$


$$= \frac{94 \Omega}{282 \Omega} * 0.4A = 0.133A^8$$

$$I_3 = \frac{R_{MN}}{R_3} * I_A$$

$$= \frac{94 \Omega}{141 \Omega} * 0.4A = 0.267A^9$$

Check $0.133 + 0.267 = 0.4$
-----------------------------

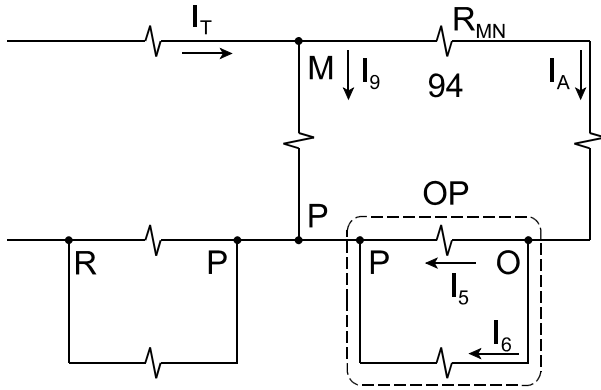
$$R_2 \parallel R_3 = 282 \parallel 141 = 94 = R_{MN}$$



$$I_5 = I_6 = \frac{R_{OP}}{R_5} * I_A$$

$$= \frac{33\Omega}{66\Omega} * 0.4A = 0.2A \quad 7$$
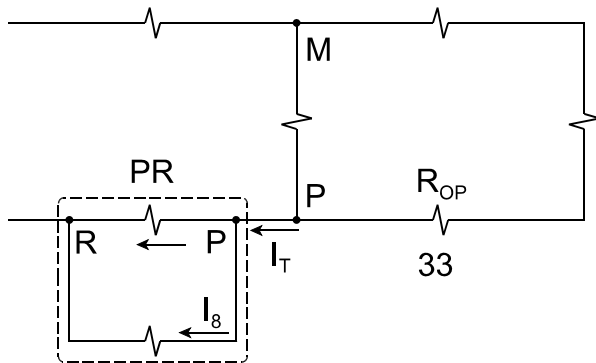
$$R_5 \parallel R_6 = 66 \parallel 66 = \frac{66}{2} = 33 = R_{OP}$$



$$I_7 = \frac{R_{PR}}{R_7} * I_T$$


$$= \frac{24\Omega}{40\Omega} * 1.2A = 0.72A \quad 5$$

$$I_8 = \frac{R_{PR}}{R_8} * I_T$$


$$= \frac{24\Omega}{60\Omega} * 1.2A = 0.48A \quad 6$$

$$R_7 \parallel R_8 = 40 \parallel 60 = 24 = R_{PR}$$

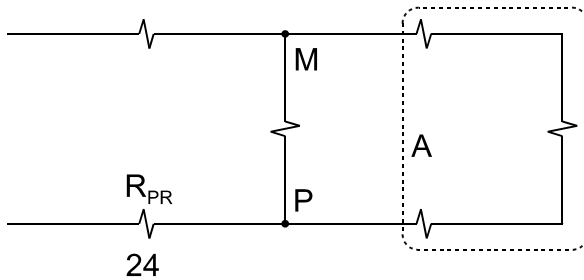Check $0.72 + 0.48 = 1.2$
---------------------------


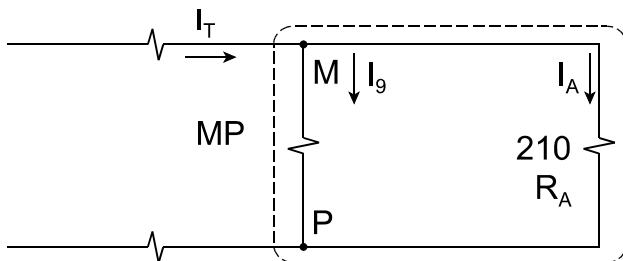
$$R_{MN} \text{ s } R_4 \text{ s } R_{OP} = 94 \text{ s } 83 \text{ s } 33 = 210 = R_A$$



$$R_A \parallel R_9 = 210 \parallel 105 = 70 = R_{MP}$$


$$I_9 = \frac{R_{MP}}{R_9} * I_T$$

$$= \frac{70\Omega}{105\Omega} * 1.2A = 0.8A \quad 3$$

$$I_4 = I_A = \frac{R_{MP}}{R_A} * I_T$$

$$= \frac{70\Omega}{210\Omega} * 1.2A = 0.4A \quad 4$$

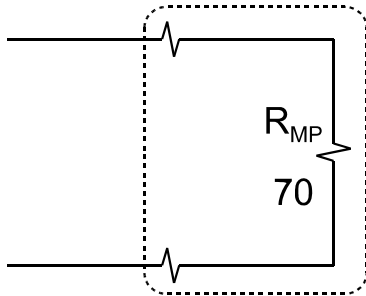Check $0.8 + 0.4 = 1.2$
-------------------------



$$R_1 \text{ s } R_{MP} \text{ s } R_{PR} = 6 \text{ s } 70 \text{ s } 24 = 100$$

$$R_T = 100 \Omega \quad ^1$$

(b)

$$I_T = \frac{V_T}{R_T} = \frac{120 \text{ V}}{100 \Omega} = 1.2 \text{ A.} \quad ^2$$

	V (V)	I (A)	R ( $\Omega$ )
<b>T</b>	<b>120</b>	$1.2^2$	$100^1$
<b>1</b>	7.2	$1.2^2$	<b>6</b>
<b>7</b>	28.8	$0.72^5$	<b>40</b>
<b>8</b>	28.8	$0.48^6$	<b>60</b>
<b>9</b>	84	$0.8^3$	<b>105</b>
<b>2</b>	37.5	$0.133^8$	<b>282</b>
<b>3</b>	37.6	$0.267^9$	<b>141</b>
<b>4</b>	33.2	$0.4^4$	<b>83</b>
<b>5</b>	13.2	$0.2^7$	<b>66</b>
<b>6</b>	$13.2^{10}$	$0.2^7$	<b>66</b>

(d)  $V_6 = I_6 * R_6 = 0.2 \text{ A} * 66 \Omega = 13.2 \text{ V} \quad ^{10}$