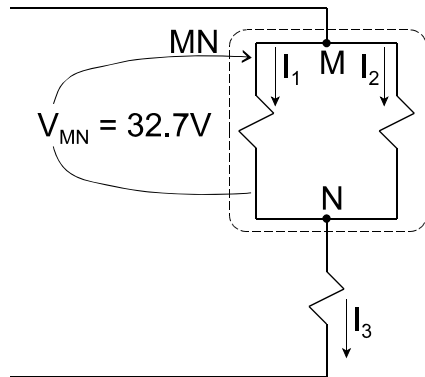


**ELECTROTECHNOLOGY  
ELTK1100  
ASSIGNMENT #3  
SOLUTIONS**

**(Series and Parallel Rules and Ohm's Law)**

1.




$$V_{MN} = V_1 = V_2 = 32.7V \quad ^5$$

$$I_1 = \frac{V_1}{R_1} = \frac{32.7V}{2k\Omega} = 16.4mA \quad ^6$$

$$I_2 = \frac{V_2}{R_2} = \frac{32.7V}{6k\Omega} = 5.5mA \quad ^7$$

$$R_1 \parallel R_2 = 2k\Omega \parallel 6k\Omega = \frac{2 * 10^3 * 6 * 10^3}{(2 * 10^3 + 6 * 10^3)}$$
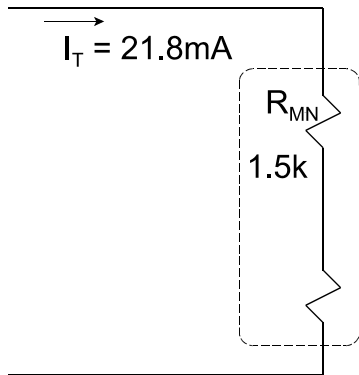
$$= \frac{1.2 * 10^7}{8 * 10^3} = 1.5k\Omega = R_{MN}$$



$$I_T = I_{MN} = I_3 = 21.8mA \quad ^3$$

$$V_{MN} = I_{MN} R_{MN} = 21.8mA * 1.5k\Omega$$

$$= 21.8 * 10^{-3} * 1.5 * 10^3 = 32.7V.$$

$$V_3 = I_3 R_3 = 21.8mA * 4k\Omega = 87.2V. \quad ^4$$


$$R_{MN} \text{ s } R_3 = 1.5k\Omega \text{ s } 4k\Omega = 1.5k\Omega + 4k\Omega = 5.5k\Omega$$

$$R_T = 5.5k\Omega \quad ^1$$

$$I_T = \frac{V_T}{R_T} = \frac{120V}{5500\Omega} = 21.8mA. \quad ^2$$

	V (V)	I (mA)	R ( $\Omega$ )
T	120	21.8 <sup>2</sup>	5.5k <sup>1</sup>
1	32.7 <sup>5</sup>	16.4 <sup>6</sup>	2k
2	32.7 <sup>5</sup>	5.5 <sup>7</sup>	6k
3	87.2 <sup>4</sup>	21.8 <sup>3</sup>	4k

2. (a)

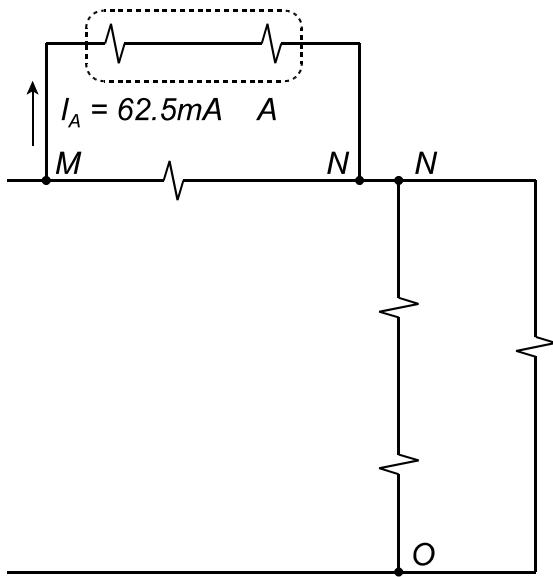


(c)  $I_A = I_1 = I_2 = 62.5 \text{ mA}$  <sup>10</sup>

$$V_1 = I_1 R_1 = 62.5 \text{ mA} * 16 \Omega = 1.0 \text{ V.}$$
 <sup>11</sup>

$$V_2 = I_2 R_2 = 62.5 \text{ mA} * 56 \Omega = 3.5 \text{ V.}$$
 <sup>12</sup>
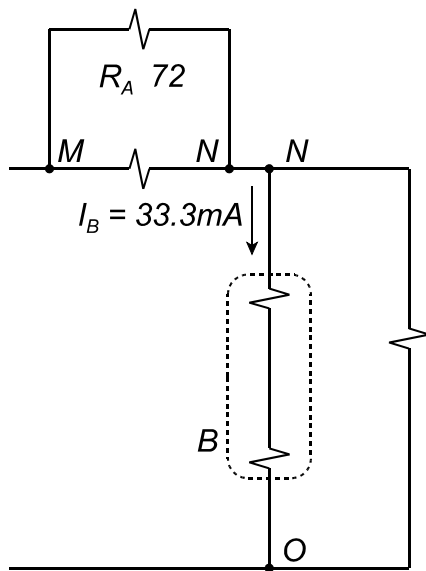
$$R_1 \text{ s } R_2 = 16 \text{ s } 56 = 72 = R_A$$




$I_B = I_4 = I_5 = 33.3 \text{ mA}$  <sup>7</sup>

$$V_4 = I_4 R_4 = 33.3 \text{ mA} * 150 \Omega = 5.0 \text{ V.}$$
 <sup>8</sup>

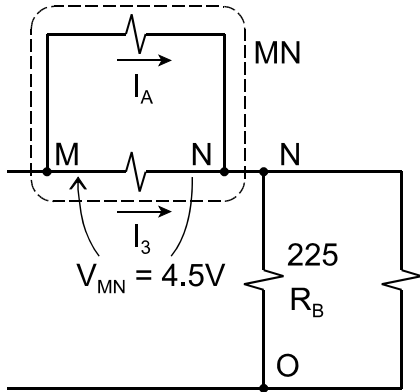(e)  $V_5 = I_5 R_5 = 33.3 \text{ mA} * 75 \Omega = 2.5 \text{ V.}$  <sup>9</sup>

$$R_4 \text{ s } R_5 = 150 \text{ s } 75 = 225 = R_B$$




$$V_{MN} = V_A = V_3 = 4.5V \quad 5$$

$$I_A = \frac{V_A}{R_A} = \frac{4.5V}{72\Omega} = 62.5mA$$

$$(d) \quad I_3 = \frac{V_3}{R_3} = \frac{4.5V}{360\Omega} = 12.5mA \quad 6$$
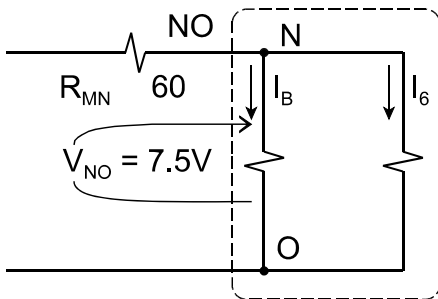
$$R_A \parallel R_3 = 72 \parallel 360 = \frac{72 * 360}{(72 + 360)} = 60 = R_{MN}$$




$$V_{NO} = V_B = V_6 = 7.5V \quad 3$$

$$I_B = \frac{V_B}{R_B} = \frac{7.5V}{225\Omega} = 33.3mA$$

$$I_6 = \frac{V_6}{R_6} = \frac{7.5V}{180\Omega} = 41.7mA \quad 4$$
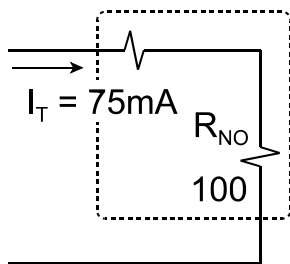
$$R_B \parallel R_6 = 225 \parallel 180 = \frac{225 * 180}{(225 + 180)} = 100 = R_{NO}$$



$$I_T = I_{MN} = I_{NO} = 75mA$$

$$V_{MN} = I_{MN} R_{MN} = 75mA * 60\Omega = 4.5V.$$

$$V_{NO} = I_{NO} R_{NO} = 75mA * 100\Omega = 7.5V.$$

$$R_{MN} s R_{NO} = 60 s 100 = 160$$


$$R_T = 160\Omega \quad 1$$

(b)


$$I_T = \frac{V_T}{R_T} = \frac{12V}{160\Omega} = 75mA. \quad 2$$

	V (V)	I (mA)	R ( $\Omega$ )
T	12	75 <sup>2</sup>	160 <sup>1</sup>
1	1 <sup>11</sup>	62.5 <sup>10</sup>	16
2	3.5 <sup>12</sup>	62.5 <sup>10</sup>	56
3	4.5 <sup>5</sup>	12.5 <sup>6</sup>	360
4	5 <sup>8</sup>	33.3 <sup>7</sup>	150
5	2.5 <sup>9</sup>	33.3 <sup>7</sup>	75
6	7.5 <sup>3</sup>	41.7 <sup>4</sup>	180


3. (a)

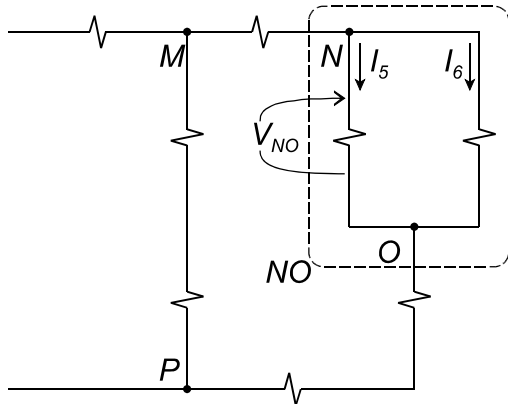
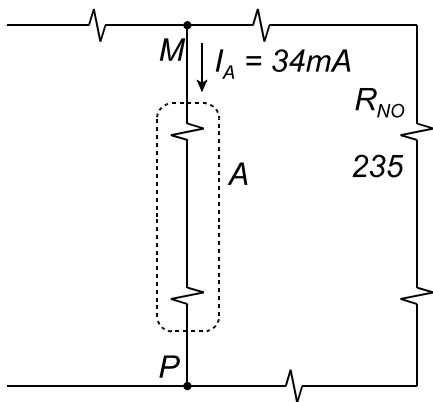
$$R_5 \parallel R_6 = 470 \parallel 470 = \frac{470}{2} = 235 = R_{NO}$$


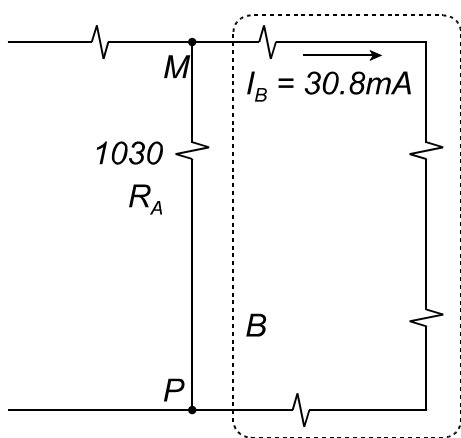
$$R_3 \text{ s } R_4 = 470 \text{ s } 560 = 1030 = R_A$$



$$R_2 \text{ s } R_{NO} \text{ s } R_7 \text{ s } R_8 = 330 \text{ s } 235 \text{ s } 470 \text{ s } 100 = 1135 = R_B$$

(c)  $V_{NO} = V_5 = V_6 = 7.24 \text{ V}$  <sup>12</sup>

$$I_5 = I_6 = \frac{V_5}{R_5} = \frac{7.24 \text{ V}}{470 \Omega} = 15.4 \text{ mA}$$
 <sup>13</sup>

$I_A = I_3 = I_4 = 34.0 \text{ mA}$ . <sup>9</sup>

$$V_3 = I_3 R_3 = 34 \text{ mA} * 470 \Omega = 16.0 \text{ V}$$
 <sup>10</sup>

(d)  $V_4 = I_4 R_4 = 34 \text{ mA} * 560 \Omega = 19.0 \text{ V}$ . <sup>11</sup>


(e)  $I_B = I_2 = I_{NO} = I_7 = I_8 = 30.8 \text{ mA}$  <sup>5</sup>

$$V_2 = I_2 R_2 = 30.8 \text{ mA} * 330 \Omega = 10.2 \text{ V}$$
 <sup>6</sup>


$$V_{NO} = I_{NO} R_{NO} = 30.8 \text{ mA} * 235 \Omega = 7.24 \text{ V}$$

$$V_7 = I_7 R_7 = 30.8 \text{ mA} * 470 \Omega = 14.5 \text{ V}$$
 <sup>7</sup>
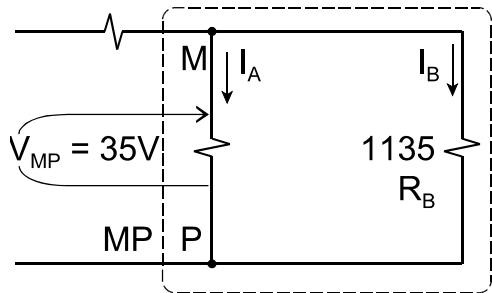
$$V_8 = I_8 R_8 = 30.8 \text{ mA} * 100 \Omega = 3.08 \text{ V}$$
 <sup>8</sup>


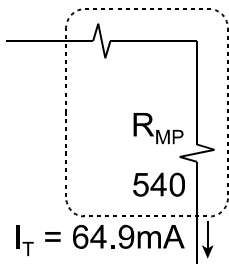
$$R_A \parallel R_B = 1030 \parallel 1135 = 540 = R_{MP}$$



$$R_1 \parallel R_{MP} = 1k \parallel 540 = 1.54k$$

$$R_T = 1.54k\Omega$$

$$(b) \quad I_T = \frac{V_T}{R_T} = \frac{100V}{1.54k\Omega} = 64.9mA$$

4.

$$I_T = 0.02A = 20mA$$

From KCL

$$I_T = I_1 + I_2 \\ \therefore I_2 = I_T - I_1 = 20mA - 16mA = 4mA$$

$$R_1 \text{ is parallel with } R_2, \\ \therefore V_1 = V_2 = 20V$$

From KVL

$$V_T = V_1 + V_3 \text{ or} \\ V_T = V_2 + V_3 \\ V_T = 20V + 16V = 36V$$

$$V_{NO} = V_A = V_B = 35V$$

$$I_A = \frac{V_A}{R_A} = \frac{35V}{1030\Omega} = 34mA$$


$$I_B = \frac{V_B}{R_B} = \frac{35V}{1135\Omega} = 30.8mA$$

$$I_T = I_1 = I_{MP} = 64.9mA$$


$$V_1 = I_1 R_1 \\ = 64.9mA * 1k\Omega = 64.9V$$

$$V_{MP} = I_{MP} R_{MP} \\ = 64.9mA * 540\Omega = 35V$$

	V (V)	I (mA)	R ( $\Omega$ )
T	100	64.9 <sup>2</sup>	1.54k <sup>1</sup>
1	64.9 <sup>4</sup>	64.9 <sup>3</sup>	1k
3	16.0 <sup>10</sup>	34.0 <sup>9</sup>	470
4	19.0 <sup>11</sup>	34.0 <sup>9</sup>	560
2	10.2 <sup>6</sup>	30.8 <sup>5</sup>	330
7	14.5 <sup>7</sup>	30.8 <sup>5</sup>	470
8	3.08 <sup>8</sup>	30.8 <sup>5</sup>	100
5	7.29 <sup>12</sup>	15.5 <sup>13</sup>	470
6	7.29 <sup>12</sup>	15.5 <sup>13</sup>	470

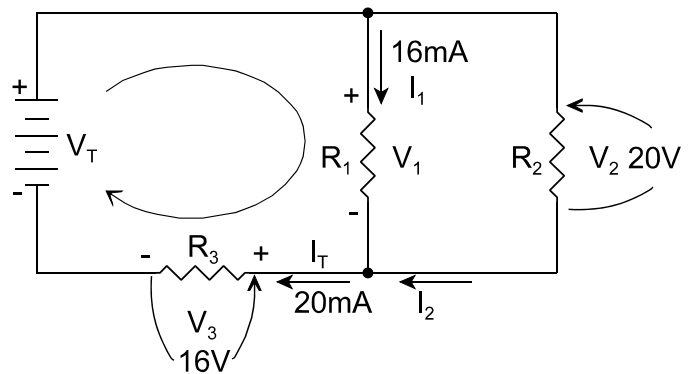



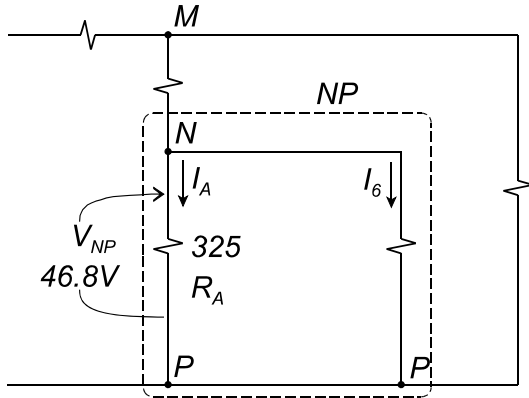


(c)  $V_{NP} = V_A = V_6 = 46.8V$  <sup>9</sup>

$$I_A = \frac{V_A}{R_A} = \frac{46.8V}{325\Omega} = 144mA$$

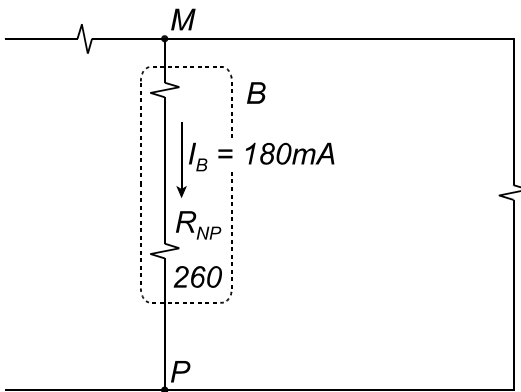(d)  $I_6 = \frac{V_6}{R_6} = \frac{46.8V}{1.3k\Omega} = 36mA$  <sup>10</sup>

$$R_A \parallel R_6 = 325 \parallel 1.3k = 260 = R_{NP}$$




$I_B = I_2 = I_{NP} = 180mA$  <sup>7</sup>

$$V_2 = I_2 R_2 = 180mA * 240\Omega = 43.2V.$$
 <sup>8</sup>

$$V_{NP} = I_{NP} R_{NP} = 180mA * 260\Omega = 46.8V.$$
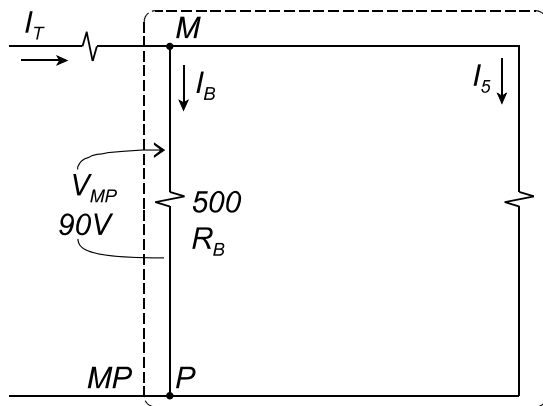
$$R_2 \parallel R_{NP} = 240 \parallel 260 = 500 = R_B$$




(c)  $V_{MP} = V_B = V_5 = 90V$  <sup>5</sup>

$$I_B = \frac{V_B}{R_B} = \frac{90V}{500\Omega} = 180mA$$

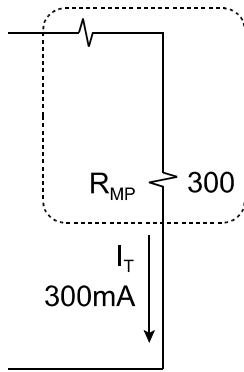(d)  $I_5 = \frac{V_5}{R_5} = \frac{90V}{750\Omega} = 120mA$  <sup>6</sup>

$$R_B \parallel R_5 = 500 \parallel 750 = 300 = R_{MP}$$



$$I_T = I_1 = I_{MP} = 300\text{mA} \quad 3$$

$$V_1 = I_1 R_1 = 300\text{mA} * 100\Omega = 30\text{V.} \quad 4$$

$$V_{MP} = I_{MP} R_{MP} = 300\text{mA} * 300\Omega = 90\text{V.}$$

$$R_1 \text{ s } R_{MP} = 100 \text{ s } 300 = 400$$

$$R_T = 400\Omega \quad 1$$

(b)

$$I_T = \frac{V_T}{R_T} = \frac{120\text{V}}{400\Omega} = 300\text{mA.} \quad 2$$

	V (V)	I (mA)	R ( $\Omega$ )
<b>T</b>	<b>120</b>	300 <sup>2</sup>	400 <sup>1</sup>
<b>1</b>	30 <sup>4</sup>	300 <sup>3</sup>	<b>100</b>
<b>5</b>	90 <sup>5</sup>	120 <sup>6</sup>	<b>750</b>
<b>2</b>	43.2 <sup>8</sup>	180 <sup>7</sup>	<b>240</b>
<b>6</b>	46.8 <sup>9</sup>	36 <sup>10</sup>	<b>1.3k</b>
<b>3</b>	28.8 <sup>12</sup>	144 <sup>11</sup>	<b>200</b>
<b>7</b>	18 <sup>13</sup>	24 <sup>15</sup>	<b>750</b>
<b>4</b>	18 <sup>13</sup>	120 <sup>14</sup>	<b>150</b>

6.

This problem exercises the rules for series/parallel circuits.

The information in **Bold** and *Italics* on the VIR chart indicates what is given.

$$G_5 = 0.5\text{S}$$

$$R_5 = \frac{1}{G_5} = \frac{1}{0.5\text{S}} = 2\Omega \quad 1$$

$$I_1 = I_7 = I_T = 8\text{A} \quad 2$$

This is obvious since they are in series with source.

Similarly


$$I_2 = I_6 = 5\text{A} \quad 3$$

By KCL on Node M

$$I_7 = I_6 + I_8$$

$$\therefore I_8 = I_7 - I_6 = 8\text{A} - 5\text{A} = 3\text{A} \quad 4$$

	V (V)	I (A)	R ( $\Omega$ )
<b>T</b>	<b>120</b>	<b>8</b>	15
<b>1</b>	<b>20</b>	8 <sup>2</sup>	2.5 <sup>9</sup>
<b>7</b>	40 <sup>5</sup>	8 <sup>2</sup>	<b>5</b>
<b>8</b>	60 <sup>5</sup>	3 <sup>4</sup>	<b>20</b>
<b>2</b>	10 <sup>5</sup>	5 <sup>3</sup>	<b>2</b>
<b>6</b>	20 <sup>6</sup>	<b>5</b>	4 <sup>9</sup>
<b>9</b>	<b>30</b>	2 <sup>8</sup>	15 <sup>9</sup>
<b>3</b>	<b>9</b>	3 <sup>7</sup>	<b>3</b>
<b>4</b>	<b>15</b>	3 <sup>7</sup>	5 <sup>9</sup>
<b>5</b>	6	3 <sup>7</sup>	2 <sup>1</sup>

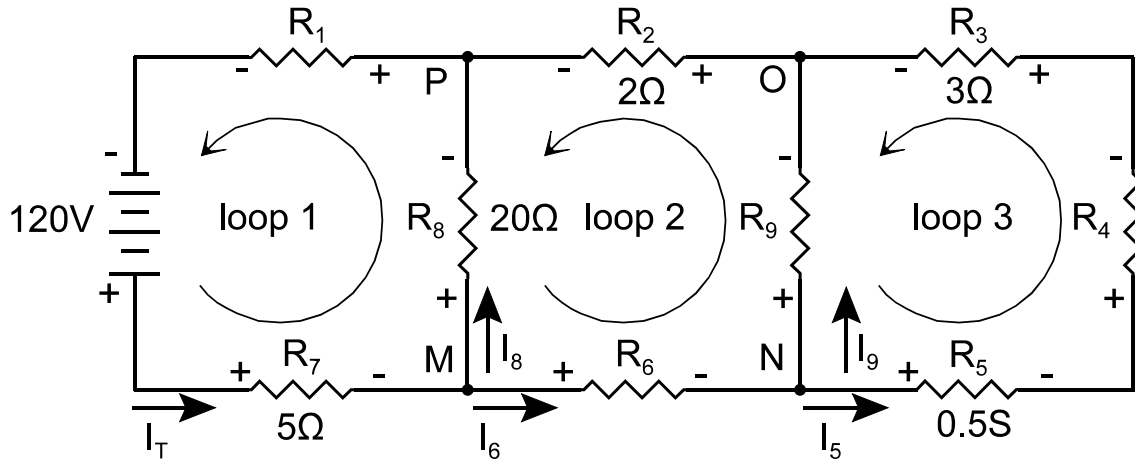

You know the current and resistance for  $R_7$ ,  $R_8$  and  $R_2$ ,  $\therefore$  you can work out their voltage drops.

$$V_7 = I_7 * R_7 = 8A * 5\Omega = 40V \quad 5$$

$$V_8 = I_8 * R_8 = 3A * 20\Omega = 60V$$

$$V_2 = I_2 * R_2 = 5A * 2\Omega = 10V$$

From KVL loop 1

$$+V_T - V_1 - V_8 - V_7 = 0$$

$$V_1 + V_8 + V_7 = V_T$$

$$20V + 60V + 40V = 120V$$

$R_1$  and  $R_7$  consume  $20V + 40V$  of potential since they are in series with the source. The left over potential  $60V$  is available for the rest of the circuit in parallel.

From KVL loop 2

$$+V_8 - V_2 - V_9 - V_6 = 0$$

$$V_6 = V_8 - V_2 - V_9 = 60V - 10V - 30V = 20V \quad 6$$

By Ohms Law

$$I_3 = I_4 = I_5 = \frac{V_3}{R_3} = \frac{9V}{3\Omega} = 3A \quad 7$$

By KCL on Node N

$$I_6 = I_5 + I_9$$

$$\therefore I_9 = I_6 - I_5 = 5A - 3A = 2A \quad 8$$


$$R_1 = \frac{V_1}{I_1} = \frac{20V}{8A} = 2.5\Omega \quad 9$$

$$R_6 = \frac{V_6}{I_6} = \frac{20V}{5A} = 4\Omega$$


$$R_9 = \frac{V_9}{I_9} = \frac{30V}{2A} = 15\Omega$$

$$R_4 = \frac{V_4}{I_4} = \frac{15V}{3A} = 5\Omega$$


7. (a)

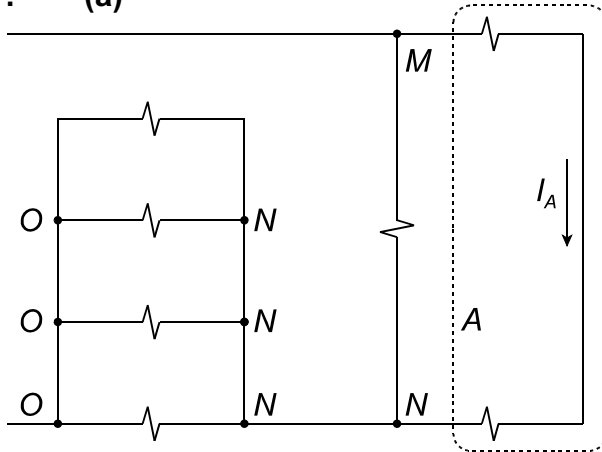
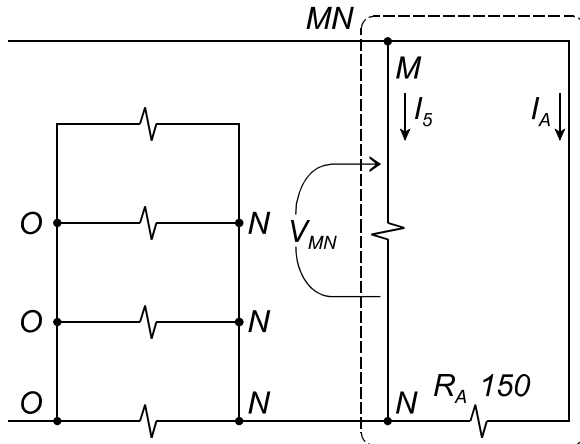
$$R_6 \parallel R_7 = 68 \parallel 82 = 150 = R_A$$


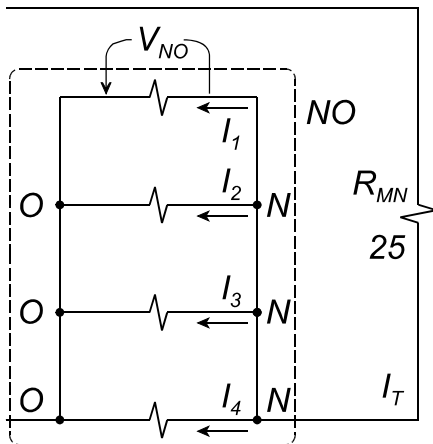
$$R_5 \parallel R_A = 30 \parallel 150 = 25 = R_{MN}$$



$$R_1 \parallel R_2 \parallel R_3 \parallel R_4 = 180 \parallel 180 \parallel 20 \parallel 180 = 15 = R_{NO}$$

or

$$180 \parallel 180 \parallel 180 = 30$$

$$30 \parallel 20 = 15 = R_{NO}$$

$$I_A = I_6 = I_7 = 0.333A \quad ^8$$

$$(c) \quad V_6 = I_6 R_6$$

$$= 0.333A * 68\Omega = 22.6V. \quad ^9$$

$$V_7 = I_7 R_7$$

$$= 0.333A * 82\Omega = 27.3V. \quad ^{10}$$

$$V_{MP} = V_5 = V_A = 50V \quad ^6$$

$$I_5 = \frac{V_5}{R_5} = \frac{50V}{30\Omega} = 1.67A \quad ^7$$


$$I_A = \frac{V_A}{R_A} = \frac{50V}{150\Omega} = 0.333A$$

$$V_{NO} = V_1 = V_2 = V_3 = V_4 = 30V \quad ^3$$

$$(d) \quad I_1 = I_2 = I_4 = \frac{V_1}{R_1} = \frac{30V}{180\Omega} = 0.167A \quad ^4$$

$$I_3 = \frac{V_3}{R_3} = \frac{30V}{20\Omega} = 1.5A \quad ^5$$

Use reciprocal rule

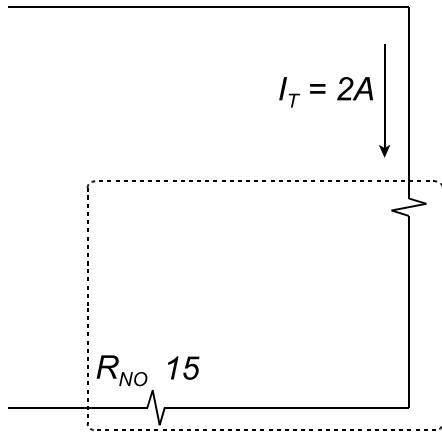

$$I_T = I_{MN} = I_{NO} = 2A$$

$$V_{MN} = I_{MN} R_{MN} = 2A * 25\Omega = 50V.$$

$$V_{NO} = I_{NO} R_{NO} = 2A * 15\Omega = 30V.$$

$$R_{NO} \text{ s } R_{MN} = 15 \text{ s } 25 = 40$$


$$R_T = 40\Omega^1$$

(b)

$$V_T = I_T * R_T = 2A * 40\Omega = 80V^2$$

	V (V)	I (A)	R ( $\Omega$ )
T	80 <sup>2</sup>	2	40 <sup>1</sup>
1	30 <sup>3</sup>	0.167 <sup>4</sup>	180
2	30 <sup>3</sup>	0.167 <sup>4</sup>	180
3	30 <sup>3</sup>	1.5 <sup>5</sup>	20
4	30 <sup>3</sup>	0.167 <sup>4</sup>	180
5	50 <sup>6</sup>	1.67 <sup>7</sup>	30
6	22.6 <sup>9</sup>	0.333 <sup>8</sup>	68
7	27.3 <sup>10</sup>	0.333 <sup>8</sup>	82

8. (a)

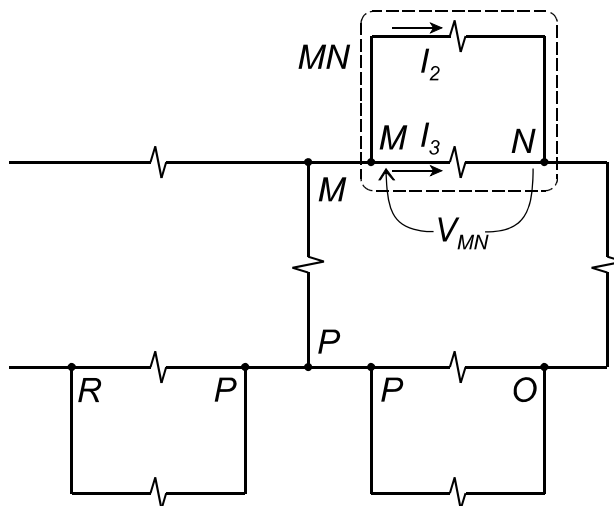


(c)

$$V_{MN} = V_2 = V_3 = 37.6V^{14}$$


$$I_2 = \frac{V_2}{R_2} = \frac{37.6V}{282\Omega} = 0.133A^{15}$$

$$I_3 = \frac{V_3}{R_3} = \frac{37.6V}{141\Omega} = 0.267A^{16}$$

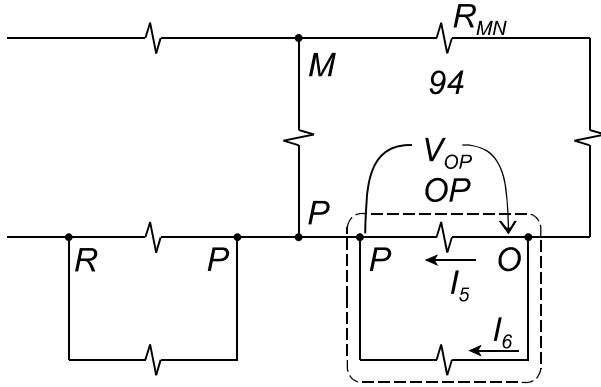
$$R_2 \parallel R_3 = 282 \parallel 141 = 94 = R_{MN}$$



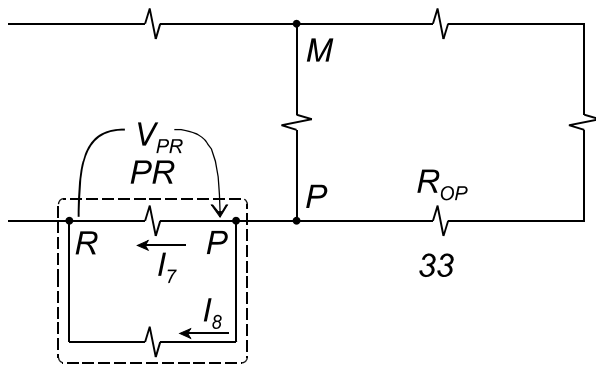
$$R_5 \parallel R_6 = 66 \parallel 66 = \frac{66}{2} = 33 = R_{OP}$$


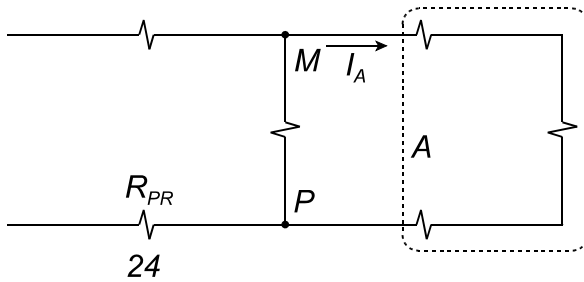
$$R_7 \parallel R_8 = 40 \parallel 60 = 24 = R_{PR}$$


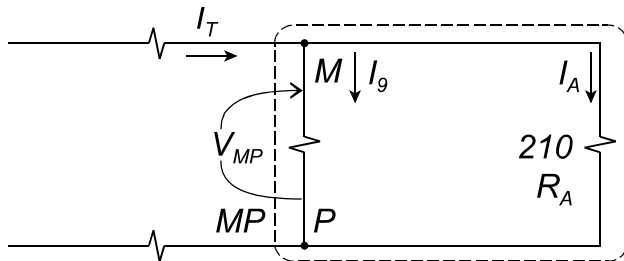
$$R_{MN} \parallel R_4 \parallel R_{OP} = 94 \parallel 83 \parallel 33 = 210 = R_A$$



$$R_A \parallel R_9 = 210 \parallel 105 = 70 = R_{MP}$$

(d)  $V_{OP} = V_5 = V_6 = 13.2V$  <sup>12</sup>

$$I_5 = I_6 = \frac{V_5}{R_5} = \frac{13.2V}{66\Omega} = 0.2A$$
 <sup>13</sup>

$$V_{PR} = V_7 = V_8 = 28.8V$$
 <sup>9</sup>

$$I_7 = \frac{V_7}{R_7} = \frac{28.8V}{40\Omega} = 0.72A$$
 <sup>10</sup>

$$I_8 = \frac{V_8}{R_8} = \frac{28.8V}{60\Omega} = 0.48A$$
 <sup>11</sup>

$$I_A = I_{MN} = I_4 = I_{OP} = 0.4A$$
 <sup>7</sup>

$$V_{MN} = I_{MN} R_{MN} = 0.4A * 94\Omega = 37.6V.$$


$$V_4 = I_4 R_4 = 0.4A * 83\Omega = 33.2V.$$
 <sup>8</sup>

$$V_{OP} = I_{OP} R_{OP} = 0.4A * 33\Omega = 13.2V.$$

$$V_{MP} = V_9 = V_A = 84V$$
 <sup>5</sup>

$$I_9 = \frac{V_9}{R_9} = \frac{84V}{105\Omega} = 0.8A$$
 <sup>6</sup>
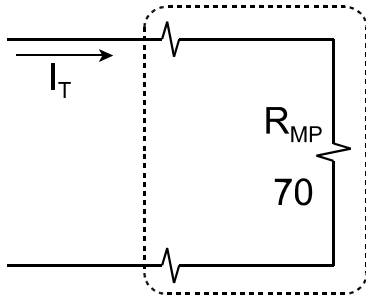
$$I_A = \frac{V_A}{R_A} = \frac{84V}{210\Omega} = 0.4A$$



$$R_1 \text{ s } R_{MP} \text{ s } R_{PR} = 6 \text{ s } 70 \text{ s } 24 = 100$$

$$R_T = 100 \Omega \quad 1$$

(b)

$$I_T = \frac{V_T}{R_T} = \frac{120 \text{ V}}{100 \Omega} = 1.2 \text{ A.} \quad 2$$

$$I_T = I_1 = I_{MP} = I_{PR} = 1.2 \text{ A} \quad 3$$

$$V_1 = I_1 R_1$$

$$= 1.2 \text{ A} * 6 \Omega = 7.2 \text{ V.} \quad 4$$

$$V_{MP} = I_{MP} R_{MP}$$

$$= 1.2 \text{ A} * 70 \Omega = 84 \text{ V.}$$

$$V_{PR} = I_{PR} R_{PR}$$

$$= 1.2 \text{ A} * 24 \Omega = 28.8 \text{ V.}$$

	V (V)	I (A)	R ( $\Omega$ )
<b>T</b>	<b>120</b>	$1.2^2$	$100^1$
<b>1</b>	$7.2^4$	$1.2^3$	<b>6</b>
<b>7</b>	$28.8^9$	$0.72^{10}$	<b>40</b>
<b>8</b>	$28.8^9$	$0.48^{11}$	<b>60</b>
<b>9</b>	$84^5$	$0.8^6$	<b>105</b>
<b>2</b>	$37.5^{14}$	$0.133^{15}$	<b>282</b>
<b>3</b>	$37.6^{14}$	$0.267^{16}$	<b>141</b>
<b>4</b>	$33.2^8$	$0.4^7$	<b>83</b>
<b>5</b>	$13.2^{12}$	$0.2^{13}$	<b>66</b>
<b>6</b>	$13.2^{12}$	$0.2^{13}$	<b>66</b>