

**ELECTROTECHNOLOGY
ELTK1100
ASSIGNMENT #7
(SOLUTIONS)**

1.

$$I_T = \frac{P_2}{V_2} = \frac{2.4 \text{ W}}{96 \text{ V}} = 25 \text{ mA} \quad 1$$

$$V_1 = V_T - V_2 = 100 \text{ V} - 96 \text{ V} = 4 \text{ V} \quad 2$$

$$R_1 = \frac{V_1}{I_1} = \frac{4 \text{ V}}{25 \text{ mA}} = 160 \Omega \quad 3$$

$$R_2 = \frac{V_2}{I_2} = \frac{96 \text{ V}}{25 \text{ mA}} = 3.84 \text{ k}\Omega \quad 4$$

$$\% \text{ Voltage Drop} = \frac{V_1}{V_T} * 100\% = \frac{4 \text{ V}}{100 \text{ V}} * 100\% = 4\%$$

	P (W)	V (V)	I (mA)	R(Ω)
T	2.5	100	25 ¹	
1	0.1	4 ²	25 ¹	160 ³
2	2.4	96	25 ¹	3840 ⁴

4%

96%

2.

$$A = \frac{\rho * l}{R} = \frac{10.37 \frac{\Omega \cdot \text{CM}}{\text{ft}} * (2 * 100 \text{ ft})}{0.37 \Omega} = 5605 \text{ CM}$$

∴ #12 6529 CM

$$R = \frac{\rho * l}{A}$$

$$\therefore A = \frac{\rho * l}{R}$$

$$\text{Actual } R \text{ #12} = 2 * 100 \text{ ft} * \frac{1.588 \Omega}{1000 \text{ ft}} = 0.3176 \Omega$$


3.

$$R = 2 * 500 \text{ ft} * \frac{0.1563 \Omega}{1000 \text{ ft}} = 0.1563 \Omega$$

or

A #2 Copper = 66373 CM
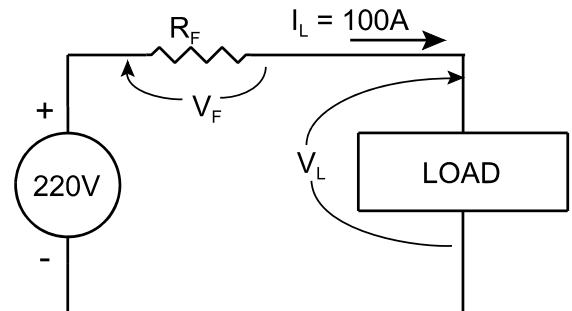
$$R = \frac{\rho * l}{A} = \frac{10.37 \frac{\Omega \cdot \text{CM}}{\text{ft}} * 2 * 500 \text{ ft}}{66373 \text{ CM}} = 0.1562 \Omega$$



	P (W)	V (V)	I (A)	R (Ω)	
T	22000	220	100		
F	1560	15.6	100	0.156	7.09%
L	20440	204.4	100		92.9%

$$V_F = I_L R_F = 100A * 0.1563\Omega = 15.6V$$

$$\% \text{ Voltage Drop} = \frac{V_F}{V_T} * 100\% = \frac{15.6V}{220V} * 100\% = 7.09\%$$

The resistivity of copper and AWG is for 20°C. If we wish to find the resistance of the conductor at a new temperature, we must use the temperature formula.

$$R_{T2} = \frac{1 + \alpha_o T_2}{1 + \alpha_o T_1} * R_{T1} = \frac{1 + 0.00427 * 70^\circ C}{1 + 0.00427 * 20^\circ C} * 0.1563\Omega = \frac{1.2989}{1.0854} * 0.1563\Omega = 0.187\Omega$$

4. (a)


$$P_L = 3 * 2.5hp * \frac{746W}{hp} + 5 * 2500W + 25 * 200W = 23095W$$

$$I_L = \frac{P_L}{V_L} = \frac{23095W}{220V} = 105A \quad 1$$

$$V_F \leq 8\% \text{ of } V_T$$

$$\therefore V_L \geq 92\% \text{ of } V_T \quad 2$$
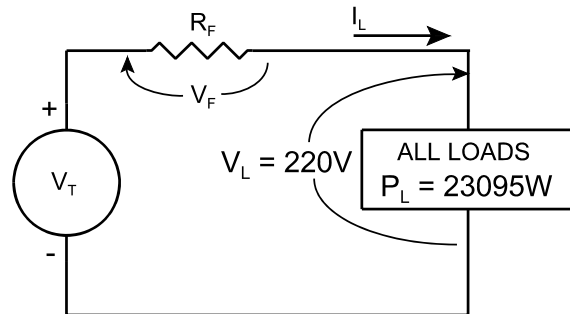
$$V_T = \frac{V_L}{92\%} = \frac{220V}{0.92} = 239.1V \quad 3$$



	P (W)	V (V)	I (A)	R (Ω)	
T	25101	239.1 ³	105 ¹		
F	2006 ⁶	19.1 ⁴	105 ¹	0.182 ⁵	8%
L	23095	220	105 ¹		92% ²

(b)

$$V_F \leq 8\% \text{ of } 239.1V = 19.1V \quad 4$$

$$R_F = \frac{V_F}{I_L} = \frac{19.1V}{105A} = 0.182\Omega \quad 5$$

$$A = \frac{\rho * l}{R_F} = \frac{10.37 \frac{\Omega \cdot CM}{ft} * 2 * 600 ft}{0.182\Omega} = 68373CM$$

$$\#1 \quad A = 83694CM$$

$$R = \frac{\rho * l}{A}$$

$$\therefore A = \frac{\rho * l}{R}$$

(c)

$$P_F = I_L^2 R_F = (105A)^2 * 0.182\Omega = 2006W \quad 6$$

5. (a)

$$P_L = 25 \text{ hp} = 25 \text{ hp} * \frac{746 \text{ W}}{\text{hp}} = 18650 \text{ W}$$


$$V_T = 240 \text{ V}$$

$$V_F \leq 2\% \text{ of } 240 \text{ V} = 4.8 \text{ V} \quad 1$$

$$V_L = V_T - V_F = 240 \text{ V} - 4.8 \text{ V} = 235.2 \text{ V} \quad 2$$

$$I_L = \frac{P_L}{V_L} = \frac{18650 \text{ W}}{235.2 \text{ V}} = 79.3 \text{ A} \quad 3$$
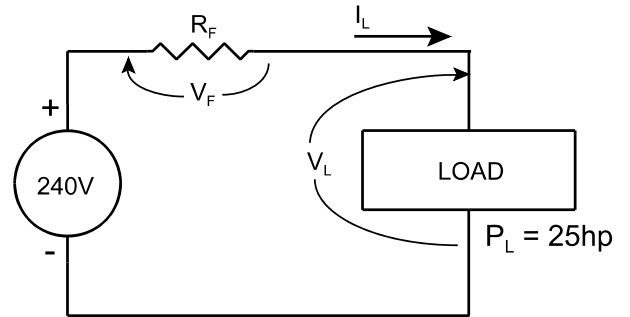
$$R_F = \frac{V_F}{I_L} = \frac{4.8 \text{ V}}{79.3 \text{ A}} = 0.06053 \Omega \quad 4$$



	P (W)	V (V)	I (A)	R (Ω)	
T	19031	240	79.3 ³		
F	381 ⁵	4.8 ¹	79.3 ³	0.06053 ⁴	2%
L	18650	235.2 ²	79.3 ³		98%

$$A = \frac{\rho * l}{R_F} = \frac{10.37 \frac{\Omega - \text{CM}}{\text{ft}} * 2 * 400 \text{ ft}}{0.06053 \Omega} = 137056 \text{ CM}$$

$$3/0 \quad A = 167810 \text{ CM}$$

$$R = \frac{\rho * l}{A}$$

$$\therefore A = \frac{\rho * l}{R}$$

(b)

$$P_F = I_L^2 R_F = (79.3 \text{ A})^2 * 0.06053 \Omega = 381 \text{ W} \quad 5$$

6.

$$P_L = 6 * 3hp * \frac{746W}{hp} = 13428W$$


$$V_T = 600V$$

$$V_F \leq 10\% \text{ of } 600V = 60V \quad 1$$

$$V_L = V_T - V_F = 600V - 60V = 540V \quad 2$$

$$I_L = \frac{P_L}{V_L} = \frac{13428W}{540V} = 24.87A \quad 3$$
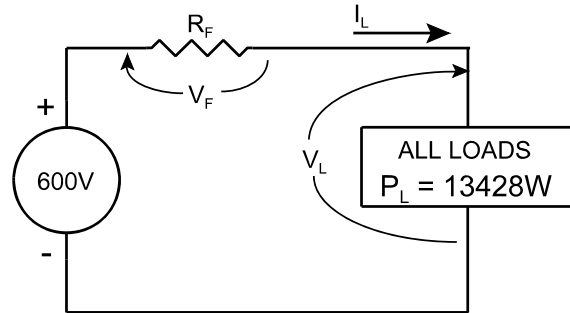
$$R_F = \frac{V_F}{I_L} = \frac{60V}{24.87A} = 2.413\Omega \quad 4$$



	P (W)	V (V)	I (A)	R (Ω)	
T	14920	600	24.87 ³		
F	1492	60 ¹	24.87 ³	2.413 ⁴	10%
L	13428	540 ²	24.87 ³		90%

1500 m of this wire must have a resistance less than 2.412 Ω . To find out which wire to use, we must calculate the $\Omega/100m$ and refer to the AWG.

$$\frac{R}{100m} = \frac{2.413\Omega}{2 * 750m}$$

$$R = \frac{2.413\Omega * 100m}{1500m} = 0.1609 \Omega$$

$$\#6 \quad 0.129 \frac{\Omega}{100m}$$

Since $V \propto R$, a smaller R ($\Omega/100m$) will ensure the voltage drop is less than 10%.

Another method is to convert the distance to ft (1m = 3.28048ft) and do the normal calculation.

$$l = 2 * 750m * 3.28048 \frac{ft}{m} = 4921ft$$

$$A = \frac{\rho * l}{R_F} = \frac{10.37 \frac{\Omega - CM}{ft} * 4921ft}{2.413\Omega} = 21148CM$$

$$\#6 \quad A = 26250CM$$