

OHM'S LAW & POWER FORMULAS PROBLEM SET

1. What resistance will cause a current of 50 mA, if the electromotive force is 12V?
2. What voltage is being applied to a circuit if the current is 500 μA and the power is 100 mW?